

III B.Tech II Semester Regular Examinations, Apr/May 2006
ANALYSIS OF LINEAR SYSTEMS
(Electrical & Electronic Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
 All Questions carry equal marks

1. (a) Distinguish between static and dynamic systems with suitable examples
- (b) Develop the force. Voltage analogous network for the system shown in figure 1 and hence develop the loop equations.

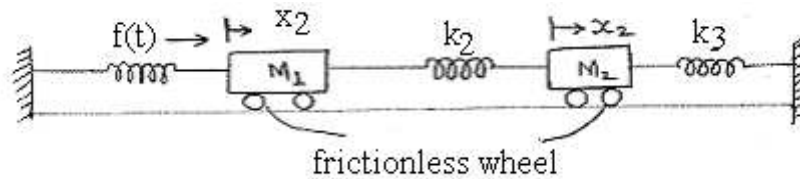


Figure 1:

- (c) Obtain the state equations of the mechanical system shown in figure 2 [4+6+6]

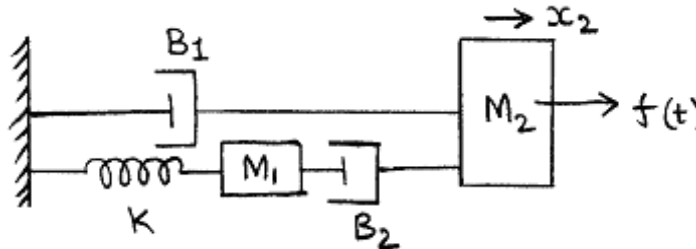


Figure 2:

2. (a) Obtain the state equations for the network shown in figure. 3 Where $i_1(t)$ and $i_2(t)$ are loop currents.
- (b) Evaluate the complete state response of the system characterized by $A = \begin{bmatrix} 2 & 0 \\ 1 & 1 \end{bmatrix}$ $B = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$ with initial state vector $X(0) = \begin{bmatrix} 1 \\ 1 \end{bmatrix}$ [8+8]
3. (a) Distinguish between unit impulse function and unit doublet function and hence develop the Laplace transform of these functions.
- (b) Find the expressions for the current $i(t)$ in a series R-L-C circuit, with $R=5\Omega$, $L=1H$, $C=\frac{1}{4} F$, when it is fed by a ramp voltage of $12 r(t-2)$. [3+3+10]
4. (a) Assuming stair case function shown in figure,4 is not repeated, and is applied to an R-L series circuit with $R=1\Omega$, $L=1H$, find the current $i(t)$.

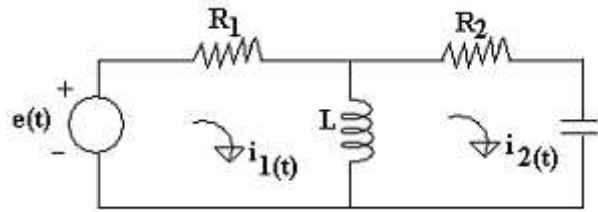


Figure 3:

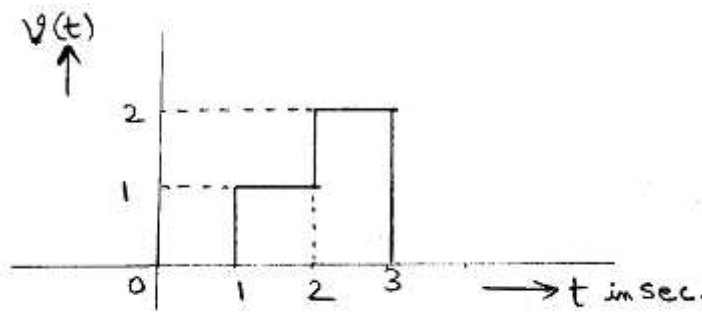


Figure 4:

- (b) Find inverse Laplace transform of $F(s) = \frac{s}{(s+1)(s+2)(s+3)}$ using convolution theorem. [8+8]
5. (a) Derive the expression for RMS value of a complex (of voltage) wave which is expressed in terms of fourier series.
- (b) A complex voltage $e(t) = 100 \sin wt + 30 \sin 3wt + 20 \sin 5wt$ where $w = 100t$. If this voltage is applied to a load of 10 ohms in series with 0.01H, find the current, average power and power factor of the circuit. [6+10]
6. (a) Find the Fourier transform of a gate function

$$G(t) = \begin{cases} 1 & \text{for } -\frac{T}{2} < t < \frac{T}{2} \\ 0 & \text{otherwise} \end{cases}$$
- (b) Find the Fourier transform of the constant signal $f(t) = A(-\infty < t < \infty)$ [8+8]
7. (a) Check whether the following polynomial is Hurwitz or not?
 $H(s) = s^4 + 2s^2 + 3s + 6$
- (b) Find the range of values of 'a' so that $H(s) = s^4 + s^3 + as^2 + s + 3$ is Hurwitz. [7+9]
8. (a) Explain how the removal of pole at infinity of an impedance $Z(s)$ can realize an element in the network.
- (b) Realize the network with the following driving point impedance function using first Foster form.
 $Z(s) = (s+2) / s(2s+5)$ [8+8]

III B.Tech II Semester Regular Examinations, Apr/May 2006
ANALYSIS OF LINEAR SYSTEMS
(Electrical & Electronic Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
 All Questions carry equal marks

1. For the mechanical system shown in figure 1.

- (a) Draw the mechanical network
 (b) Develop the electric analogous circuits and the corresponding state-variable models. [4+6+6]

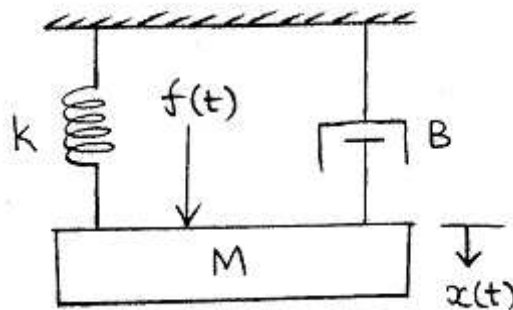


Figure 1:

2. (a) Write matrix state equation for the circuit shown in figure.2

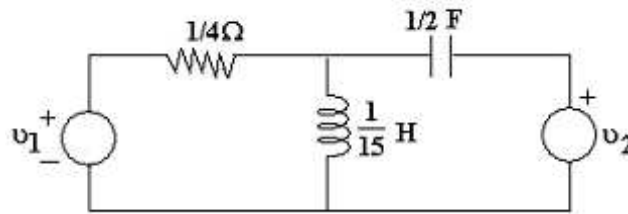


Figure 2:

(b) Find the complete state response of the system

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -1 & 0 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 1 \end{bmatrix} u(t) \text{ and } \begin{bmatrix} x_1(0) \\ x_2(0) \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix} \quad [8+8]$$

3. A series R-C ckt. With $R = 1\Omega$, $C = 1\text{F}$ is fed by a voltage of non-periodic waveform shown in figure 3. Find the response $i(t)$ using Laplace transform approach. [16]
4. (a) Determine the current in a series R-L circuit driven by a square wave, periodic function shown in figure 4 With $R=1\Omega$, $L=1\text{H}$.

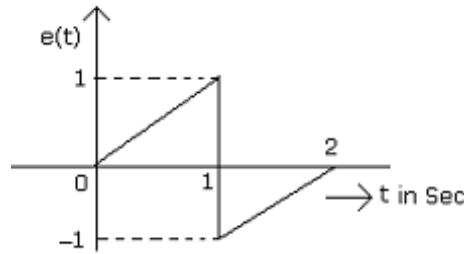


Figure 3:

- (b) Find the convolution of $h(t)=t$, and $f(t)=e^{-at}$ for $t > 0$, using the inverse Laplace transform of $H(s)$ $F(s)$. [8+8]

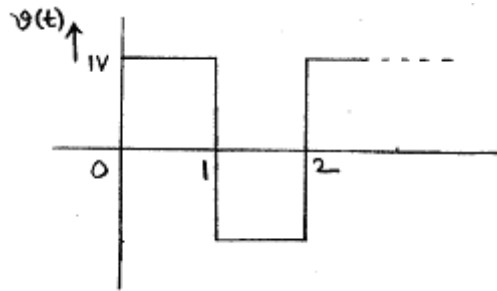


Figure 4:

5. (a) Derive the expression for RMS value of a complex (of voltage) wave which is expressed in terms of fourier series.
 (b) A complex voltage $e(t) = 100 \sin w t + 30 \sin 3wt + 20 \sin 5 wt$ where $w = 100t$. If this voltage is applied to a load of 10 ohms in series with 0.01H, find the current, average power and power factor of the circuit. [6+10]
6. (a) State and explain Parseval's theorem.
 (b) Derive the expression for Fourier transform of unit step function. [7+9]
7. (a) Check whether the following polynomial is Hurwitz or not?
 $P(s) = 2s^4 + 5s^3 + 6s^2 + 2s + 1$
 (b) " All driving point immittances of passive networks are positive real functions". Substantiate the statement.
 (c) State the analytical tests to be considered for a polynomial to check whether it is a positive real function or not? [7+5+4]
8. (a) Explain how the removal of pole at infinity of an impedance $Z(s)$ can realize an element in the network.
 (b) Realize the network with the following driving point impedance function using first Foster form.
 $Z(s) = (s+2) / s(2s+5)$ [8+8]

III B.Tech II Semester Regular Examinations, Apr/May 2006
ANALYSIS OF LINEAR SYSTEMS
(Electrical & Electronic Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
 All Questions carry equal marks

1. (a) For the figure 1 shown below , draw the mechanical system. And hence write the equilibrium equations
- (b) Draw the electrical analogous circuits for the mechanical system shown in figure2 [8+8]

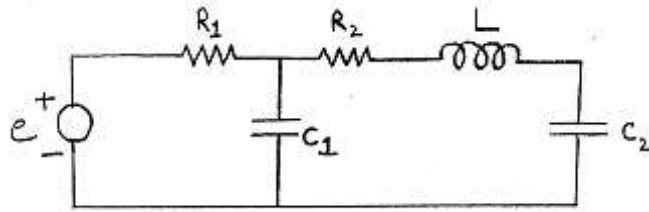


Figure 1:

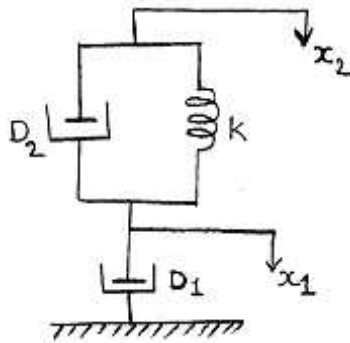


Figure 2:

2. (a) Evaluate the state transition matrix for the system characterized by $A = \begin{bmatrix} 8 & -8 & -2 \\ 4 & -3 & -2 \\ 3 & -4 & 1 \end{bmatrix}$
- (b) Develop the state equations of the following network. figure3 [8+8]
3. (a) A pulse voltage of 3V between 1 to 2 sec. is applied to a series R-L circuit with $R=3\ \Omega$, $L=1H$, Find the current $i(t)$.
- (b) Find the current $i(t)$ in a series R-L-C circuit with $R=3\ \Omega$, $L=1H$, $C=\frac{1}{2}F$ when it is driven by an impulse voltage of $\delta(t-2)$. [6+10]

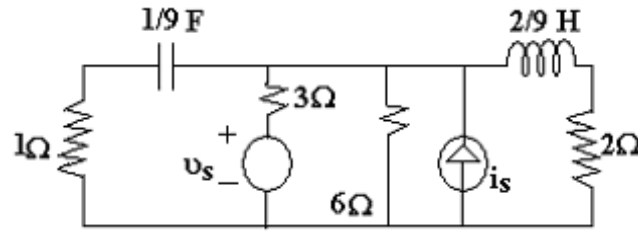


Figure 3:

4. (a) Find the inverse Laplace transform of the periodic signal shown in figure 4.
- (b) When an unit impulse voltage is applied to a certain network, the output voltage is $V_o(t) = 4u(t) - 4u(t-2)$ Volts. Find and sketch $V_o(t)$ if the input voltage is $2u(t-1)$ Volts. [8+8]

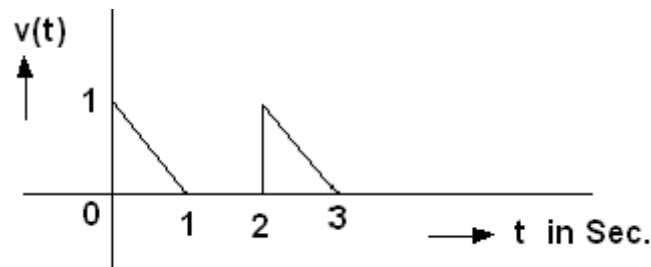


Figure 4:

5. (a) Derive the expression for Average power of a complex wave which is expressed in terms of fourier series.
- (b) The current waveform shown in figure 5 is applied to a circuit containing 0.01 micro-farads in parallel with 1 kilo ohm with a range of frequency 13 to 14 kHz. Find the average power delivered to the resistor. [6+10]

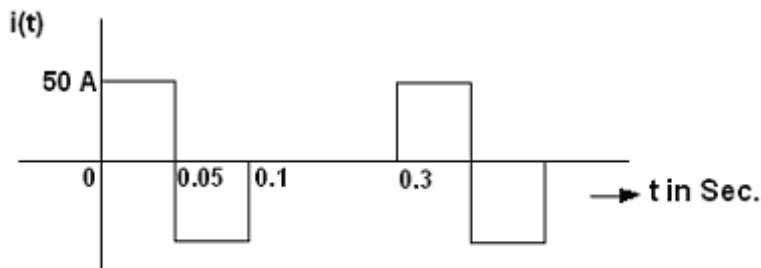


Figure 5:

6. (a) State and explain Parseval's theorem.
- (b) Derive the expression for Fourier transform of unit step function. [7+9]
7. (a) Check whether the following polynomial is Hurwitz or not?
 $P(s) = 2s^4 + 5s^3 + 6s^2 + 2s + 1$

- (b) “ All driving point immittances of passive networks are positive real functions”. Substantiate the statement.
- (c) State the analytical tests to be considered for a polynomial to check whether it is a positive real function or not? [7+5+4]
8. (a) Explain how the removal of pole at infinity of an impedance $Z(s)$ can realize an element in the network.
- (b) Realize the network with the following driving point impedance function using first Foster form.
- $Z(s) = (s+2) / s(2s+5)$ [8+8]

★ ★ ★ ★ ★

III B.Tech II Semester Regular Examinations, Apr/May 2006
ANALYSIS OF LINEAR SYSTEMS
(Electrical & Electronic Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
 All Questions carry equal marks

1. For the following mechanical rotational system, shown in figure1.
- (a) Draw the mechanical network and write the equilibrium equations.
- (b) Develop electric analogous circuits and write the corresponding equations. [8+8]

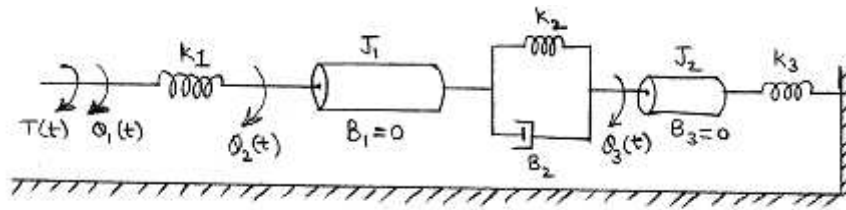


Figure 1:

2. (a) Develop the state equations of the following network: figure 2
- (b) Derive the expression to find the solution of the state equations $X(t) = A x(t) + B u(t)$ with $x(0) = x_0$ using state Transition Matrix approach. [8+8]

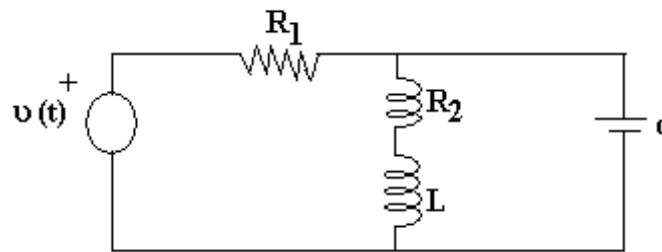


Figure 2:

3. (a) The transfer function of an armature controlled d.c. motor relating the output speed to the input armature voltage is given by $H(s) = \frac{0.03}{(s+0.06)}$. Determine the output speed as a function of time when the armature is to a step voltage of 240V.
- (b) State and explain what is meant by Gate functions and hence develop the Laplace transforms of it. [8+8]

4. (a) Assuming stair case function shown in figure,3 is not repeated, and is applied to an R-L series circuit with $R=1\Omega$, $L=1H$, find the current $i(t)$.
 (b) Find inverse Laplace transform of $F(s) = \frac{s}{(s+1)(s+2)(s+3)}$ using convolution theorem. [8+8]

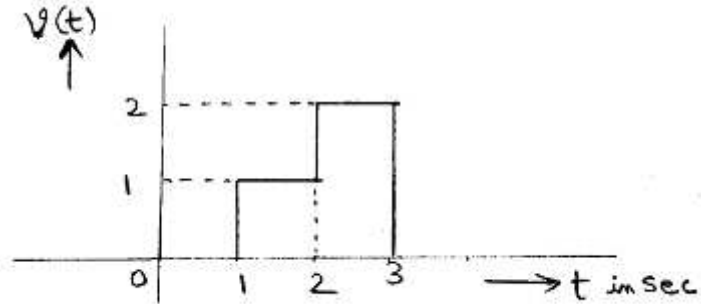


Figure 3:

5. (a) Obtain the trigonometric Fourier series representation of voltage waveform shown in figure. 4

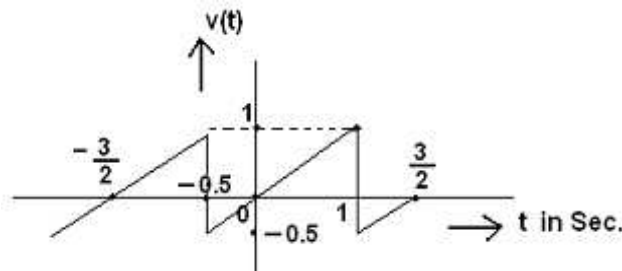


Figure 4:

- (b) Find the exponential form of the Fourier series for the following waveform shown in figure. 5 [8+8]

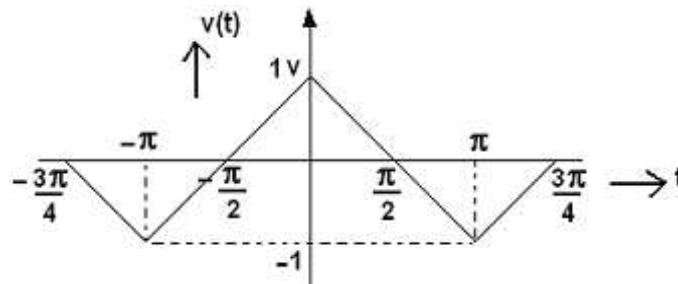


Figure 5:

6. (a) State and explain the properties of Fourier Transform.
 (b) Define Signum function and hence develop the expression for Fourier transform of it. [8+8]

7. (a) Check whether the following polynomial is Hurwitz or not?
 $H(s) = s^4 + 2s^2 + 3s + 6$
- (b) Find the range of values of 'a' so that $H(s) = s^4 + s^3 + as^2 + s + 3$ is Hurwitz.
[7+9]
8. The driving point impedance of a one port L- C network is given by
 $Z(s) = 5s(s^2 + 4)/(s^2 + 1)(s^2 + 9)$
Obtain the first and second Foster form of equivalent networks. [8+8]
