

**III B.Tech II Semester Regular Examinations, Apr/May 2006**  
**VLSI SYSTEMS DESIGN**  
**(Information Technology)**

**Time: 3 hours**

**Max Marks: 80**

**Answer any FIVE Questions**  
**All Questions carry equal marks**

\*\*\*\*\*

1. Implement the following gates with n-MOS transistors only and explain its working
  - (a) 3 Input NAND gate.
  - (b) Inverter. [8+8]
2. Explain working principal of n-MOS transistor with sketches of its structure. [16]
3. Design a stick diagram for CMOS logic shown below.  
 $Y = (AB + CD)^1$  [16]
4. Design a layout for CMOS 3-input NOR gate. [16]
5. Explain the delay calculation procedure for CMOS inverter. [16]
6. Draw the structure of carry select adder and explain its working principle. [16]
7. Explain how Architecture driven voltage scaling technique reduces the power consumption of the design. [16]
8. Clearly explain about event driven simulation with suitable example. [16]

\*\*\*\*\*

**III B.Tech II Semester Regular Examinations, Apr/May 2006**  
**VLSI SYSTEMS DESIGN**  
**(Information Technology)**

**Time: 3 hours****Max Marks: 80**

**Answer any FIVE Questions**  
**All Questions carry equal marks**

\*\*\*\*\*

1. Implement the following logic functions using CMOS logic
  - (a)  $Y = \{A.B.C.D\}^1$
  - (b)  $Y = \{A + B + C + D\}^1$  [8+8]
2. An n-MOS transistor is operating in the triode region with the following parameters  $\mu_n Cox = 90\mu A/V^2$  W/L ( ratio) = 100  $V_{gs} = 4V$ ,  $V_{tn} = 1V$ ,  $V_{ds} = 2V$ . Find its drain current & drain -Source resistance. [16]
3. Design a stick diagram for CMOS EX-NOR gate. [16]
4. (a) What do you mean by layout of a component?  
(b) Draw neat layout diagram for NMOS transistor [8+8]
5. Define faults of a Digital circuit and Explain about stuck at 0 /1 faulty models [16]
6. Give a complete table of the barrel shifter's possible operations. List all possible combinations of top and bottom inputs and the resulting operation. [16]
7. Clearly discuss about power distribution and clock distribution routing procedure. [16]
8. Sketch the architecture of the kitchen timer chip and explain about its architecture design. [16]

\*\*\*\*\*

**III B.Tech II Semester Regular Examinations, Apr/May 2006**  
**VLSI SYSTEMS DESIGN**  
**(Information Technology)**

**Time: 3 hours**

**Max Marks: 80**

**Answer any FIVE Questions**  
**All Questions carry equal marks**

\*\*\*\*\*

1. Implement the following logic functions using CMOS logic
  - (a)  $Y = \{(A + B)(C + D)\}^1$
  - (b)  $Y = \{AB + C\}^1$  [8+8]
2. Explain about different computer aided design tools used in designing Integrated Circuits. [16]
3. Explain with neat sketches CMOS fabrication using P - well process. [16]
4. (a) What do you mean by layout of a component?  
(b) Draw neat layout diagram for NMOS transistor [8+8]
5. Define faults of a Digital circuit and Explain about stuck at 0 /1 faulty models [16]
6. Draw the structure of carry select adder and explain its working principle. [16]
7. Clearly explain how ASM chart is a useful abstraction for register transfer design. [16]
8. With suitable example explain any one of the scheduling algorithm [16]

\*\*\*\*\*

**III B.Tech II Semester Regular Examinations, Apr/May 2006**  
**VLSI SYSTEMS DESIGN**  
**(Information Technology)**

**Time: 3 hours**

**Max Marks: 80**

**Answer any FIVE Questions**  
**All Questions carry equal marks**

\*\*\*\*\*

1. Implement the following gates with CMOS Logic and explain its working
  - (a) 2 Input NAND gate.
  - (b) 3 Input NOR gate. [8+8]
2. Name different IC fabrication technologies with suitable examples. [16]
3. Design a stick diagram for CMOS, EX-OR and Inverter gates. [16]
4. Implement EX-OR and EX-NOR gates using static complementary logic. [16]
5.
  - (a) Explain the power calculation procedure of CMOS inverter.
  - (b) Explain the speed - power product significance of a logic family. [8+8]
6. Discuss clearly about the following system Design principles.
  - (a) Pipelining
  - (b) Data-paths [8+8]
7. Explain clearly the detailed routing phase of the floor planning of the chip with few examples by considering all constraints. [16]
8. Sketch the architecture of the kitchen timer chip and explain about its architecture design. [16]

\*\*\*\*\*