

**II B.Tech II Semester Supplementary Examinations,
November/December 2005
DIGITAL CIRCUITS DESIGN AND APPLICATION
(Bio-Medical Engineering)**

Time: 3 hours

Max Marks: 80

**Answer any FIVE Questions
All Questions carry equal marks**

1. (a) A symmetrical square wave whose average value is zero has a peak-to-peak amplitude of 20V and a period of $2 \mu\text{sec}$. This waveform is applied to a low-pass circuit whose upper 3-dB frequency is $\frac{1}{2\pi}$ MHz. Calculate and sketch the steady state output waveform. [8]
- (b) The input Voltage V_i to the two-level clipper shown in figure 1 varies linearly from 0 to 150V. Sketch the output voltage V_o to the same time scale as the input voltage. Assume ideal diodes. [8]

 


Figure 1:

2. Consider a collector-coupled astable multi using npn transistors. The circuit and device parameters are $V_{cc} = 15 \text{ V}$, $R_c = 3\text{K}$, $R_1 = 40\text{K}$, $R_2 = 20\text{K}$, $h_{fe} = 30$, $\gamma_{bb} = 0$, $I_{CBO} = 0$, and all forward-biased junction voltages may be neglected. calculate and plot the waveforms at the base and collector of one transistor. If the multi is oscillate at a frequency of 5 KHz, what is the value of the coupling capacitance? [16]
3. (a) Draw the functional schematic of a 555 timer and explain its operation . [10]
(b) Explain any two applications of 555 timer in detail. [6]
4. (a) Encode the decimal numbers into

- i) $(56)_{10} = (\quad)_{\text{Graycode}}$
- ii) $(20.305)_{10} = (\quad)_{\text{excess-3code}}$
- iii) $(32.89)_{10} = (\quad)_{\text{BCD code}}$

[6]

- (b) Simplify the logic expression using K.map .
 $f = ABC + B\overline{C}D + \overline{A}BC$
and realize 'f' using NAND gates only. [10]
5. (a) Using tabulation procedure find set of prime implements and obtain a minimal expression for the following.
 $f(w, x, y, z) = \Sigma(1, 5, 6, 7, 9, 13, 14, 15, 17, 18, 19, 20, 25, 29, 30)$ [10]
(b) Draw the block schematic of 4x1 MUX and give its truth table. [6]
6. (a) Design a full adder with minimum number of NAND gates. [8]
(b) Draw the logic diagram of 1 to 4 line demultiplexer and explain its operation. [8]
7. (a) Design a modulo-6 counter using NAND gates and JK flip flops. [8]
(b) Draw C-MOS inverter and explain its operation and give typical input and output voltages of $V_{DD} = 5V$ [8]
8. Write short notes on any three topics: [5+5+6=16]
(a) LED Displays
(b) Dot matrix display
(c) PLL ICs
(d) TTL gates
