

**II B.Tech II Semester Supplementary Examinations, Nov/Dec 2005**  
**PULSE & DIGITAL CIRCUITS**  
 ( Common to Electronics & Instrumentation Engineering and Electronics &  
 Control Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
 All Questions carry equal marks

\*\*\*\*\*

1. (a) The input to a high pass RC circuit is periodic and trapezoidal as indicated below. Assume that the time constant  $RC$  is large compared with either  $T_1$  or  $T_2$ . Find and sketch the steady state output if  $RC=10T_1=10T_2$ . (figure 1)

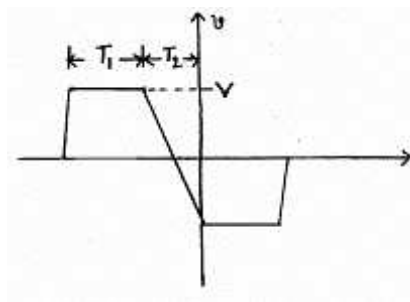


Figure 1:

[10]

- (b) Derive the expression for percentage tilt  $P$  of a square wave output of a RC high pass circuit. [6]
2. (a) Discuss the effect of Diode characteristics on clamping voltage. [6]
- (b) A symmetrical square wave of 100 Hz whose peak to peak amplitude is 20V is applied to the circuit shown in figure 2 below. Sketch the steady state output waveform indicating clearly the voltage levels and time constants. Assume that the diode has zero cut-in voltage,  $100\Omega$  forward resistance in infinite reverse resistance. [10]

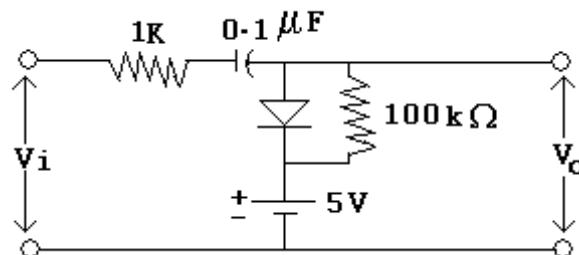


Figure 2:

3. (a) Explain how transistor can be used as a switch in the circuit, under what condition a transistor is said to be 'OFF' and 'ON' respectively. [6]  
 (b) A germanium transistor is operated at room temperature in the CE configuration. The supply voltage is 6 V, the collector-circuit resistance is  $200\ \Omega$  and the base current is 20 percent higher than the minimum value required to drive the transistor into saturation. Assume the following transistor parameters:  
 $I_{co} = -5\ \mu\text{A}$ ,  $I_{EO} = -2\ \mu\text{A}$ ,  $h_{FE} = 100$ , and  $r_{bb'} = 250\ \Omega$ . Find  $V_{BE}(\text{Sat})$  and  $V_{CE}(\text{Sat})$ . [10]
4. (a) Draw the circuit diagram of an astable multi and explain its operation. [10]  
 (b) A collector-coupled astable multi uses n-p-n transistors with  $h_{FE}(\text{min}) = 30$ . The parameter values are:  
 $R_1 = R_2 = 50\ \text{K}\Omega$  and  $C_1 = C_2 = 0.1\ \mu\text{F}$ .  
 Find the pulse width, period and frequency of the output. [6]
5. With reference to voltage sweeps explain the following terms: [16]
  - (a) Sweep speed
  - (b) Linearity of sweep
  - (c) Sweep stability
  - (d) Recovery time.
6. (a) How astable multivibrator can be synchronized? Illustrate with waveforms. [8]  
 (b) A symmetrical astable multivibrator using transistor operates from 10V supply has a period of 1msec. Triggering pulses of spacing 750 microsec are applied to one base through a small capacitor from a high-impedance source. Find the minimum triggering pulse amplitude required to achieve 1:1 synchronization. [8]
7. (a) Explain the operation of multiple input unidirectional sampling gate using diodes. [6]  
 (b) Illustrate with circuit diagram, the operation of the above with a number of control voltage inputs. [6]  
 (c) Give an alternate circuit whose output is not sensitive to upper level of control voltage. [4]
8. Explain the recovery and loading considerations in blocking oscillator and the effect of providing damping. Give an alternate circuit to have pulse period independent of RL. [16]

\*\*\*\*\*