

## III B.Tech II Semester Supplementary Examinations,

November/December 2005

## VLSI DESIGN

( Common to Electronics &amp; Communication Engineering and Electronics &amp; Telematics)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

1. (a) Clearly explain the body effect of the MOSFET.  
(b) Clearly explain about channel length modulation of the MOSFET. [8+8]
2. With neat sketches explain BICMOS fabrication in an n-well process. [16]
3. What is a stick diagram and explain about different symbols used for components in stick diagram. [16]
4. Design a layout diagram for CMOS inverter. [16]
5. Two nMOS inverters are cascaded to drive a capacitive load  $C_L = 16C_g$  as shown in Figure 1. Calculate the pair delay  $V_{in}$  to  $V_{out}$  in terms of  $\tau$  for the given data.

Inverter -A

$$L_{P,U} = 16\lambda, W_{P,U} = 2\lambda, L_{P,d} = 2\lambda, W_{P,d} = 2\lambda$$

Inverter -B

$$L_{P,U} = 2\lambda, W_{P,U} = 2\lambda, L_{P,d} = 2\lambda, W_{P,d} = 8\lambda \quad [16]$$

 


Figure 1:

6. Using PLA Implement Half-adder circuit. [16]
7. Explain the following processes in the ASIC design flow.  
(a) Post - layout timing simulation.  
(b) Post synthesis simulation. [8+8]
8. With neat sketches explain the electron lithography process. [16]

\*\*\*\*\*

**III B.Tech II Semester Supplementary Examinations,  
November/December 2005  
VLSI DESIGN**

( Common to Electronics & Communication Engineering and Electronics & Telematics)

Time: 3 hours

Max Marks: 80

**Answer any FIVE Questions  
All Questions carry equal marks**

\*\*\*\*\*

1. (a) Find  $g_m$  and  $r_{ds}$  for an n-channel transistor with  
 $V_{GS} = 1.2V$ ;  $V_{tn} = 0.8V$ ;  $W/L = 10$ ;  $\mu_n C_{ox} = 92 \mu A/V^2$  and  $V_{DS} = V_{eff} + 0.5V$   
 The out put impedance constant.  $\lambda = 95.3 \times 10^{-3} V^{-1}$   
 (b) Explain the term Figure of merit of a MOS Transistor. [10+6]
2. (a) Compare between CMOS an bipolar technologies.  
 (b) With neat sketches explain nMOS fabrication process. [8+8]
3. Design a stick diagram for p-MOS Ex-OR gate. [16]
4. Explain with suitable examples how design the layout of a gate to maximize performance and minimize area. [16]
5. Calculate on resistance of the circuit shown in Figure 1 from  $V_{DD}$  to GND. If n-channel sheet resistance  $R_{sn} = 10^4 \Omega$  per square and p-channel sheet resistance  $R_{sp} = 3.5 \times 10^4 \Omega$  per square. [16]

 


Figure 1:

6. With neat sketches explain the architecture of PAL. [16]
7. (a) Define the term DFT and explain about it.  
 (b) Explain any one test procedure to test sequential logic. [8+8]

8. Mention different growth technologies of the thin oxides and explain about any one technique. [16]

\*\*\*\*\*

## III B.Tech II Semester Supplementary Examinations,

November/December 2005

## VLSI DESIGN

( Common to Electronics &amp; Communication Engineering and Electronics &amp; Telematics)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

1. (a) Drive an equation for  $R_{DS}$  of an n-channel enhancement MOSFET in linear region.
- (b) For the Figure 1 shown, plot the trans conductance as a function of  $V_{DS}$

 


Figure 1:

[10+6]

2. (a) Compare between CMOS and bipolar technologies.
- (b) With neat sketches explain nMOS fabrication process. [8+8]
3. Design a stick diagram for the CMOS logic shown below  $Y = \overline{(A + B).C}$  [16]
4. Design a layout diagram for nMOS inverter. [16]
5. Calculate the gate capacitance value of  $5\mu m$  technology minimum sized transistor with gate to channel capacitance value is  $4 \times 10^{-4} pF/\mu m^2$ . [16]
6. Implement 4-2 Encoder using PROM. [16]
7. What are the different report files that are provided by the place and route tool and discuss clearly about each report file. [16]
8. Explain about the following Die bondings.
  - (a) Eutectic die bonding.
  - (b) Epoxy die bonding. [8+8]

\*\*\*\*\*

## III B.Tech II Semester Supplementary Examinations,

November/December 2005

## VLSI DESIGN

( Common to Electronics &amp; Communication Engineering and Electronics &amp; Telematics)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

1. (a) Explain with neat sketches the Drain and Transfer characteristics of n-channel enhancement MOSFET.  
(b) With neat sketches explain the transfer characteristics of a CMOS inverter. [10+6]
2. With neat sketches explain how Diodes and Resistors are fabricated in pMOS process. [16]
3. What is a stick diagram and explain about different symbols used for components in stick diagram. [16]
4. Design a layout diagram for the CMOS logic shown below  $Y = \overline{(A + B + C)}$  [16]
5. Two nMOS inverters are cascaded to drive a capacitive load  $C_L = 14C_g$  as shown in Figure 1. Calculate the pair delay  $V_{in}$  to  $V_{out}$  in terms of  $\tau$  for the given data.

Inverter -A

$$L_{P,U} = 12\lambda, W_{P,U} = 4\lambda, L_{P,d} = 1\lambda, W_{P,d} = 1\lambda$$

Inverter -B

$$L_{P,U} = 4\lambda, W_{P,U} = 4\lambda, L_{P,d} = 2\lambda, W_{P,d} = 8\lambda \quad [16]$$

 


Figure 1:

6. Explain about the following gate array based ASICS
  - (a) Channel gate arrays
  - (b) Channel less gate arrays
  - (c) Structured gate arrays

[5+5+6]

7. What are the inputs that are provided to the synthesis tool? And explain completely about synthesis process in the ASIC design. [16]
8. With neat sketches explain the oxidation process in the IC fabrication process. [16]

\*\*\*\*\*