

**IV B.Tech I Semester Regular Examinations, November 2005**  
**VLSI DESIGN**  
**(Bio-Medical Engineering)**

**Time: 3 hours****Max Marks: 80**

**Answer any FIVE Questions**  
**All Questions carry equal marks**

\*\*\*\*\*

1. A MOS Transistor in the active region measured to have a drain current of  $20 \mu\text{A}$  when  $V_{DS} = V_{\text{eff}}$ . When  $V_{DS}$  is increased by  $0.5\text{V}$ ,  $I_D$  increases to  $23 \mu\text{A}$ . Estimate the out impedance  $r_{ds}$ , and the out impedance constant  $\lambda$ . [16]
2. (a) With neat sketches explain CMOS fabrication using p-well process.  
(b) With neat sketches explain pMOS fabrication process. [10+6]
3. What is a stick diagram and explain about different symbols used for components in stick diagram. [16]
4. Explain with suitable examples how design the layout of a gate to maximize performance and minimize area. [16]
5. Derive equations for rise time and fall time estimation of CMOS inverter circuit. [16]
6. With neat sketch clearly explain the architecture of a PLA. [16]
7. What are the inputs that are provided to the synthesis tool? And explain completely about synthesis process in the ASIC design. [16]
8. Explain about the following Die bandings.
  - (a) Eutectic die bonding.
  - (b) Epoxy die bonding. [8+8]

\*\*\*\*\*

IV B.Tech I Semester Regular Examinations, November 2005  
VLSI DESIGN  
(Bio-Medical Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

1. (a) Find  $g_m$  and  $r_{ds}$  for an n-channel transistor with  
 $V_{GS} = 1.2V$ ;  $V_{tn} = 0.8V$ ;  $W/L = 10$ ;  $\mu_n C_{ox} = 92\mu A/V^2$  and  $V_{DS} = V_{eff}$ .  
 The out put impedance constant.  $\lambda = 95.3 \times 10^{-3} V^{-1}$   
 (b) Define the term Threshold voltage of MOSFET and explain its significance.  
[10+6]
2. With neat sketches explain BICMOS fabrication in an n-well process. [16]
3. Design a stick diagram for two input CMOS NAND and NOR gates. [16]
4. Explain with suitable examples how design the layout of a gate to maximize performance and minimize area. [16]
5. Calculate on resistance of the circuit shown in Figure 1 from  $V_{DD}$  to GND. If n-channel sheet resistance  $R_{sn} = 10^{-4} \Omega$  per square and p-channel sheet resistance  $R_{sp} = 1.5 \times 10^4 \Omega$  per square. [16]

 


Figure 1:

6. With neat sketch explain clearly the architecture of the PROM. [16]
7. Clearly explain each step of high level design flow of an ASIC. [16]
8. Explain about the following Die bandings.  
 (a) Eutectic die bonding.

(b) Epoxy die bonding.

[8+8]

\*\*\*\*\*

IV B.Tech I Semester Regular Examinations, November 2005  
VLSI DESIGN  
(Bio-Medical Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

1. A MOS Transistor in the active region measured to have a drain current of  $20 \mu\text{A}$  when  $V_{DS} = V_{eff}$ . When  $V_{DS}$  is increased by  $0.5\text{V}$ ,  $I_D$  increases to  $23 \mu\text{A}$ . Estimate the out impedance  $r_{ds}$ , and the out impedance constant  $\lambda$ . [16]
2. (a) Compare between CMOS and bipolar technologies.  
(b) With neat sketches explain nMOS fabrication process. [8+8]
3. Design a stick diagram for the NMOS logic shown below  $Y = \overline{(A + B).C}$  [16]
4. Design a layout diagram for pMOS inverter. [16]
5. Calculate on resistance of the circuit shown in Figure 1 from  $V_{DD}$  to GND. If n-channel sheet resistance  $R_{sn} = 10^4 \Omega$  per square and p-channel sheet resistance  $R_{sp} = 4.5 \times 10^4 \Omega$  per square. [16]

 


Figure 1:

6. Implement 4-2 Encoder using PROM. [16]
7. Mention about various types of simulators used in ASIC design flow and clearly discuss about the significance of each simulator. [16]
8. With neat sketches explain Atmospheric- pressure chemical vapor deposition method. [16]

\*\*\*\*\*

**IV B.Tech I Semester Regular Examinations, November 2005**  
**VLSI DESIGN**  
**(Bio-Medical Engineering)**

**Time: 3 hours****Max Marks: 80**

**Answer any FIVE Questions**  
**All Questions carry equal marks**

\*\*\*\*\*

1. (a) With neat sketches explain the formation of the inversion layer in P-channel Enhancement MOSFET.  
(b) An NMOS Transistor is operated in the triode region with the following parameters  $V_{GS} = 4V$ ;  $V_{tn} = 1V$ ;  $V_{DS} = 2V$ ;  $W/L = 100$ ;  $\mu_n C_{ox} = 90 \text{ A/V}^2$ . Find its drain current and drain source resistance. [8+8]
2. With neat sketches explain how Diodes and Resistors are fabricated in pMOS process. [16]
3. Design a stick diagram for n-MOS Ex-NOR gate. [16]
4. Design a layout diagram for two input CMOS NAND gate. [16]
5. Calculate the gate capacitance value of  $2\mu m$  technology minimum size transistor with gate to channel capacitance value is  $8 \times 10^{-4} pF/\mu m^2$ . [16]
6. (a) What are the advantages and disadvantages of the reconfiguration.  
(b) Mention different advantages of Anti fuse Technology. [8+8]
7. Name different layout analysis and design tools? Explain the job of these tools. [16]
8. With neat sketches explain Atmospheric- pressure chemical vapor deposition method. [16]

\*\*\*\*\*