

IV B.Tech I Semester Supplementary Examinations, November 2005
INDUSTRIAL ELECTRONICS
(Electronics & Control Engineering)

Time: 3 hours**Max Marks: 80**

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Draw a two stage (identical) direct coupled amplifier and explain its principle of operation.
(b) What is drift? Explain. [10+6]
2. (a) Explain in detail the principle of obtaining a regulated power supply.
(b) What is a controlled series voltage regulator? Give its block diagram.
(c) Tabulate the differences between
 - i. Shunt and series regulators.
 - ii. Zener shunt regulator and transistorized shunt regulator. [5+5+6]
3. An LM 217 IC voltage regulator, is to produce an output of 8V with $I_L(\text{max}) = 100\text{mA}$. Calculate the suitable resistances for the output and select an appropriate supply voltage and also determine the device power dissipation. [16]
4. (a) List the major applications of thyristors ?
(b) Explain the theory and operation of SCR using suitable figures.
(c) Draw the load-voltage waveforms for thyristor circuit with dc input. [5+5+6]
5. Describe the operation of a single phase, two-pulse, mid-point converter with relevant voltage and current waveforms. Discuss how each SCR is subjected to a reverse voltage equal to double the supply voltage in case turns ratio from primary to each secondary is unity. [16]
6. Design a snubber circuit and explain its operation and give its applications. [16]
7. (a) Explain the principle and operation of SCR alarm circuit.
(b) Explain the speed control of induction motor using triac. [8+8]
8. (a) Explain the theory and principle of dielectric heating.
(b) List various Industrial applications of dielectric heating. [8+8]
