

II B.Tech I Semester Supplementary Examinations, November 2006
SWITCHING THEORY & LOGIC DESIGN

(Common to Electrical & Electronic Engineering, Electronics & Communication Engineering, Computer Science & Engineering, Electronics & Instrumentation Engineering, Information Technology, Electronics & Control Engineering, Computer Science & Systems Engineering, Electronics & Telematics and Electronics & Computer Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Write the following binary numbers in signed 1's complement form and signed 2's complement form using 16 bit registers.
 - i. +1001010
 - ii. -11110000
 - iii. -11001100.1
 - iv. +100000011.111
- (b) Perform $N_1 + N_2$, $N_1 + (-N_2)$ for the following 8 bit numbers expressed in a 2's complement representation. Verify your answers by using decimal addition and subtraction
 - i. $N_1 = 00110010$, $N_2 = 11111101$
 - ii. $N_1 = 10001110$, $N_2 = 00001101$

[10+6]

2. (a) Simplify the function using Karnaugh map method
 $F(A, B, C, D) = \sum(4, 5, 7, 12, 14, 15) + \sum d(3, 8, 10)$.
- (b) Give three possible ways to express the function
 $F = \overline{A} \overline{B} \overline{D} + \overline{A} \overline{B} \overline{C} \overline{D} + \overline{A} B D + A B \overline{C} D$ with eight or less literals. [8+8]
3. (a) Derive Boolean expression for a 2 input Ex-NOR gate to realize with two input NOR gates, without using complemented variables and draw the circuit.
- (b) Redraw the given circuit (figure 3b) after simplification.

 


Figure 3b

[8+8]

4. Design a PLA to realize the following three logic functions and show the internal connections

$$\begin{aligned}
F_1(a, b, c, d, e) &= \bar{a}\bar{b}\bar{d} + \bar{b}c\bar{d} + \bar{a}bcd\bar{e} \\
F_2(a, b, c, d, e) &= \bar{a}be + \bar{b}c\bar{d}e \\
F_3(a, b, c, d, e) &= \bar{a}\bar{b}\bar{d} + \bar{b}c\bar{d}e + \bar{a}bcd
\end{aligned}
\tag{16}$$

5. (a) Define a combinational system and a sequential system and how does they differ from each other
- (b) Draw the schematic circuit of “Master-slave J-K-Flip-Flop” using NAND gates and explain its operation with the help of Truth-Table.

[8+8]

6. Design a sequential circuit with two D- flipflops A and B and one input x. When x=0, the state of the circuit remains the same. When x=1, the circuit goes through the state transitions from 00 to 01 to 11 to 10 back to 00 and repeats. [16]
7. Find the equivalence partition for the given machine. Show a standard form of the corresponding reduced machine.

PS	NS,Z	
	X=0	X=1
A	F,0	B,1
B	G,0	A,1
C	B,0	C,1
D	C,0	B,1
E	D,0	A,1
F	E,1	F,1
G	E,1	G,1

[16]

8. (a) Construct an ASM chart for a decimal system that counts the number of people in a room. People enter the room from one door, with a photocell that changes a signal x from 1 to 0, when the light is interpreted. They leave the room from a second door, with a similar photocell with a signal y. Both x and y are synchronized with a clock but they may stay on or off for more than one clock pulse period. The data processor subsystem consists of an up down counter with a display of its contents.
- (b) Design a four bit counter with synchronous clear with a diagram specified in the data processor

[8+8]
