

**II B.Tech I Semester Regular Examinations, November 2006**  
**SWITCHING THEORY & LOGIC DESIGN**  
 ( Common to Electrical & Electronic Engineering, Electronics &  
 Instrumentation Engineering, Bio-Medical Engineering, Electronics &  
 Control Engineering, Electronics & Computer Engineering and  
 Instrumentation & Control Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
 All Questions carry equal marks

\*\*\*\*\*

1. (a) Generate Hamming code for the given 11 bit message 10001110101 and rewrite the entire message with Hamming code. [8]
- (b) The binary numbers listed have a sign bit in the left most position and, if negative numbers are in 2's complement form. Perform the arithmetic operations indicated and verify the answers. [4 × 2 = 8]
  - i. 101011 + 111000
  - ii. 001110 + 110010
  - iii. 111001 - 001010
  - iv. 101011 - 100110
2. (a) Reduce the following Boolean Expressions [8]
  - i.  $AB + A(B + C) + B'(B + D)$
  - ii.  $A + B + A'B'C$
  - iii.  $A'B + A'BC' + A'BCD + A'BC'D'E$
  - iv.  $ABEF + AB(EF)' + (AB)'EF$
- (b) Obtain the Dual of the following Boolean expressions. [8]
  - i.  $x'yz + x'yz' + xy'z' + xy'z$
  - ii.  $x'yz + xy'z' + xyz + xyz'$
  - iii.  $x'z + x'y + xy'z + yz$
  - iv.  $x'y'z' + x'yz' + xy'z' + xy'z + xyz'$
3. (a) Simplify the Boolean expression using K-map  $F = (ABCD\bar{D}) + (A) + (AB\bar{D}) + (\bar{D})(\bar{A}\bar{B}\bar{C})$ . [8]
- (b) Reduce the following function using K-map and identify the prime implicant and non prime implicant.  $F = \sum m(2, 3, 6, 7, 10, 11, 12)$ . [8]
4. (a) Design a Excess-3 adder using 4-bit parallel binary adder and logic gates.
- (b) Draw the logic diagram of a single bit comparator. [12+6]
5. (a) Derive the PLA programming table for the combinational circuit that squares a 3 bit number.

- (b) For the given 3-input, 4-output truth table of a combinations circuit, tabulate the PAL programming table for the circuit. [8+8]

Inputs			Output			
x	y	z	A	B	C	D
0	0	0	0	1	0	0
0	0	1	1	1	1	1
0	1	0	1	0	1	1
0	1	1	0	1	0	1
1	0	0	1	0	1	0
1	0	1	0	0	0	1
1	1	0	1	1	1	0
1	1	1	0	1	1	1

6. (a) Find a modulo-6 gray code using k-Map & design the corresponding counter.  
 (b) Compare synchronous & Asynchronous. [8+8]
7. A clocked sequential circuit is provided with a single input x and single output Z. Whenever the input produce a string of pulses 1 1 1 or 0 0 0 and at the end of the sequence it produce an output  $Z = 1$  and overlapping is also allowed.
- (a) Obtain State - Diagram.  
 (b) Also obtain state - Table.  
 (c) Find equivalence classes using partition method & design the circuit using D - flip-flops. [4+4+8]
8. (a) Draw the ASM chart for the following state transistion, start from the initial state  $T_1$ , then if  $xy=00$  go to  $T_2$ , if  $xy=01$  go to  $T_3$ , if  $xy=10$  go to  $T_1$ , other wise go to  $T_3$ .  
 (b) Show the exit paths in an ASM block for all binary combinations of control variables x, y and z, starting from an initial state. [8+8]

\*\*\*\*\*

**II B.Tech I Semester Regular Examinations, November 2006**  
**SWITCHING THEORY & LOGIC DESIGN**  
 ( Common to Electrical & Electronic Engineering, Electronics &  
 Instrumentation Engineering, Bio-Medical Engineering, Electronics &  
 Control Engineering, Electronics & Computer Engineering and  
 Instrumentation & Control Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
 All Questions carry equal marks

\*\*\*\*\*

1. (a) Perform the following using BCD arithmetic. [2 × 4 = 8]
  - i.  $7129_{10} + 7711_{10}$
  - ii.  $8124_{10} + 8127_{10}$
- (b) Convert the following. [4 × 2 = 8]
  - i.  $AB_{16} = ( \quad )_{10}$
  - ii.  $1234_8 = ( \quad )_{10}$
  - iii.  $10110011_2 = ( \quad )_{10}$
  - iv.  $772_{10} = ( \quad )_{16}$
2. (a) Simplify the following Boolean expressions to minimum no. of literals. [8]
  - i.  $x'y' + xy + x'y$
  - ii.  $xy' + y'z' + x'z'$
  - iii.  $x'? + xy + xz' + xy'z'$
  - iv.  $(x + y)(x + y')$
- (b) Obtain the complement of the following Boolean expressions. [8]
  - i.  $AB + A(B + C) + B'(B + D)$
  - ii.  $A + B + A'B'C$
  - iii.  $A'B + A'BC' + A'BCD + A'BC'D'E$
  - iv.  $ABEF + ABE'F' + A'B'EF$
3. Apply Branching method to simplify the following function  
 $F(A, B, C, D) = \prod M(0, 1, 4, 5, 9, 11, 13, 15, 16, 17, 25, 27, 28, 29, 31)d(20, 21, 22, 30).$   
[16]
4. (a) Design a Excess-3 adder using 4-bit parallel binary adder and logic gates.  
 (b) Draw the logic diagram of a single bit comparator. [12+6]
5. (a) Find the function  $f(x_1, x_2, x_3, x_4)$  realized by each of the threshold networks shown in the figure 5(a)i, 5(a)ii, 5b. [8+8]

i.

 


Figure 5(a)i

ii.

 


Figure 5(a)ii

(b)

 


Figure 5b

6. (a) Give the design of 4 bit Ring counter and explain it with the waveforms. Also give the application of this ring counter.
- (b) Design a modulo-9 counter T flipflops with preset and clear inputs. [8+8]
7. A clocked sequential circuit is provided with a single input  $x$  and single output  $Z$ . Whenever the input produces a string of pulses 1 1 1 or 0 0 0 and at the end of the sequence it produces an output  $Z = 1$  and overlapping is also allowed.
  - (a) Obtain State - Diagram.
  - (b) Also obtain state - Table.
  - (c) Find equivalence classes using partition method & design the circuit using D - flip-flops. [4+4+8]
8. For the ASM chart given 8:

 


Figure 8

- (a) Draw the state diagram.
- (b) Design the control unit using D flip-flops and a decoder. [8+8]

\*\*\*\*\*

**II B.Tech I Semester Regular Examinations, November 2006**  
**SWITCHING THEORY & LOGIC DESIGN**  
 ( Common to Electrical & Electronic Engineering, Electronics &  
 Instrumentation Engineering, Bio-Medical Engineering, Electronics &  
 Control Engineering, Electronics & Computer Engineering and  
 Instrumentation & Control Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
 All Questions carry equal marks

\*\*\*\*\*

1. Convert the following to Decimal and then to Octal.
  - (a)  $4234_{16}$
  - (b)  $125F_{16}$
  - (c)  $10010011_2$
  - (d)  $10111111_2$
  - (e)  $392_{10}$
  - (f)  $779_{10}$  [3+3+3+3+2+2]
2. (a) Simplify the following expressions and implement them with NAND gate circuits. [8]
  - i.  $AB' + ABD + ABD' + A'C'D' + A'BC'$
  - ii.  $BD + BCD' + AB'C'D'$
- (b) Obtain the Dual of the following Boolean expressions.
  - i.  $AB + A(B + C) + B'(B + D)$
  - ii.  $A + B + A'B'C$  [4]
- (c) Obtain the complement of the following Boolean expressions.
  - i.  $A'B + A'BC' + A'BCD + A'BC'D'E$
  - ii.  $ABEF + ABE'F' + A'B'EF$  [4]
3. Minimise on the map the five variable function.  
 $F = \sum m(0, 1, 4, 5, 6, 13, 14, 15, 22, 24, 25, 28, 29, 30, 31).$  [16]
4. (a) Design a 32:1 Multiplexer using two 16:1 and 2:1 Multiplexers.  
 (b) Design a circuit to convert Excess-3 code to BCD code Using a 4-bit Full adder. [8+8]
5. (a) Given a 32 x 8 Rom chip with an enable input, show the external connection necessary to construct a 128 x 8 Rom with four chips and a decoder.

- (b) Tabulate the PLA programming table for the four Boolean functions listed below

$$A(x,y,z) = \varepsilon(1, 2, 4, 6)$$

$$B(x,y,z) = \varepsilon(0, 1, 6, 7)$$

$$C(x,y,z) = \varepsilon(2,6)$$

$$D(x,y,z) = \varepsilon(1, 2, 3, 5, 7). \quad [8+8]$$

6. (a) Compare synchronous & Asynchronous circuits  
 (b) Design a Mod-6 synchronous counter using J-K flip flops. [6+10]
7. A clocked sequential circuit is provided with a single input x and single output Z. Whenever the input produce a string of pulses 1 1 1 or 0 0 0 and at the end of the sequence it produce an output Z = 1 and overlapping is also allowed.
- (a) Obtain State - Diagram.  
 (b) Also obtain state - Table.  
 (c) Find equivalence classes using partition method & design the circuit using D - flip-flops. [4+4+8]
8. (a) Draw the ASM chart for the following state transistion, start from the initial state  $T_1$ , then if xy=00 go to  $T_2$ , if xy=01 go to  $T_3$ , if xy=10 go to  $T_1$ , other wise go to  $T_3$ .  
 (b) Show the exit paths in an ASM block for all binary combinations of control variables x, y and z, starting from an initial state. [8+8]

\*\*\*\*\*

**II B.Tech I Semester Regular Examinations, November 2006**  
**SWITCHING THEORY & LOGIC DESIGN**  
 ( Common to Electrical & Electronic Engineering, Electronics &  
 Instrumentation Engineering, Bio-Medical Engineering, Electronics &  
 Control Engineering, Electronics & Computer Engineering and  
 Instrumentation & Control Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
 All Questions carry equal marks

\*\*\*\*\*

1. (a) Generate Hamming code for the given 11 bit message 10010110101 and rewrite the entire message with Hamming code. [8]  
 (b) The binary numbers listed have a sign bit in the left most position and, if negative numbers are in 2's complement form. Perform the arithmetic operations indicated and verify the answers. [4×2=8]
  - i. 101011 + 111001
  - ii. 001111 + 110010
  - iii. 111001 - 011010
  - iv. 101111 - 100110
2. (a) Draw the logic diagram using only two input NAND gates to implement the following expression. [8]  
 $(AB + A'B')(CD' + C'D)$   
 (b) Obtain the complement of the following Boolean expressions.
  - i.  $B'C'D + (B + C + D)' + B'C'D'E$
  - ii.  $AB + (AC)' + (AB + C)$  [4]
- (c) Obtain the dual of the following Boolean expressions.
  - i.  $A'B'C' + A'BC' + AB'C' + ABC'$
  - ii.  $AB + (AC)' + AB'C$  [4]
3. (a) Differentiate prime implicant and non prime implicant, essential prime implicant and non essential prime implicant. [8]  
 (b) Reduce the following function using K- map and identify prime implicants and essential prime implicants  $F = \sum m(0, 1, 2, 3, 6, 7, 13, 15)$  [8]
4. (a) Design a 32:1 Multiplexer using two 16:1 and 2:1 Multiplexers.  
 (b) Design a circuit to convert Excess-3 code to BCD code Using a 4-bit Full adder. [8+8]
5. Write a brief note on:
  - (a) Architecture of PLDS
  - (b) Capabilities and the limitations of threshold gates. [8+8]



6. (a) Compare synchronous & Asynchronous circuits  
 (b) Design a Mod-6 synchronous counter using J-K flip flops. [6+10]
7. A clocked sequential circuit with simple input  $x$  and single output  $Z$  produce an output  $Z = 1$  whenever the input  $x$  completes the sequence 1 0 1 1 and overlapping is allowed.  
 (a) Obtain its state - diagram.  
 (b) Obtain its minimal state - table and design the circuit with D - Flip-Flops. [8+8]
8. (a) For the given state-diagram of a control circuit 8 obtain ASM chart.  
 (b) Design the circuit using multiplexers. [8+8]

 


Figure 8

\*\*\*\*\*