



Answer any FIVE Questions

(Each question carries 14 marks)

Q. No.	Stem of the question	M	L	CO	PO
Unit-I					
1. a)	Explain the difference between MOSFET, BJT and IGBT	7	1	1	1
b)	Explain the working of MOS Turn off Thyristor	7	2	1	1
Unit-II					
2. a)	Explain in detail about Series Resonant Inverters with unidirectional switches	7	1	2	1
b)	The series resonant inverter has $L_1 = L_2 = L = 50\mu\text{H}$, $C = 6\mu\text{F}$, $R = 2\Omega$, $V_s = 220\text{V}$, frequency of output voltage is of $f_o = 7\text{KHz}$. Turn off time of thyristor is $t_q = 10\text{mS}$. Find i) the available circuit turn off time (toff), ii) Maximum permissible frequency (fmax) iii) V_{pp} (peak to peak capacitor voltage iv) The peak load current (I_p)	7	4	2	2
Unit-III					
3. a)	Explain in detail about M type ZCS resonant converter with waveforms and circuit diagram	7	1	3	2
b)	The ZCS Resonant Converter delivers a maximum power of $P_L = 400\text{MW}$ at $V_o = 4\text{V}$. The supply voltage is $V_s = 12\text{V}$. The maximum operating frequency is $f_{\text{max}} = 50\text{kHz}$. Find the value of L and C. Assume that the intervals t_1 and t_3 are very small and $x = 1.5(I_m/I_o)$	7	5	3	3
Unit-IV					
4. a)	Explain the operation of ZVS resonant converter with neat diagram and output waveforms	10	4	4	4
b)	List out the applications of Multilevel inverters	4	1	4	1
Unit-V					
5. a)	Explain the Principle of operation of Flying Capacitor multilevel inverter with neat diagram and output waveforms	10	1	5	6
b)	What is the need of Resonant converter	4	1	5	5
a. Unit-I b. Unit-II					
6. a)	Explain Brief about DC side voltage control in rectifier	4	3	1	1
b)	Explain in detail about Parallel Resonant Inverter with neat diagram and output waveforms	10	4	2	3
a. Unit-III b. Unit-IV					
7. a)	Explain in detail about L type ZCS resonant converter	4	3	1	3
b)	Discuss the principle, operation and features of 3-level diode clamped multilevel Inverter	10	1	2	4
a. Unit-V b. Unit-I/II/III/IV/V					
8. a)	Explain in detail about Class E Resonant rectifier with neat diagram and output waveforms	7	1	2	5
b)	Give the advantages and disadvantages with comparing multilevel inverter, diode clamped multilevel inverter, Firing Capacitor multilevel inverter and Cascade H bridge multilevel inverter.	7	2	3	3

M: Marks; L: Bloom's Taxonomy Level; CO: Course Outcome; PO: Programme Outcome



MAHATMA GANDHI INSTITUTE OF TECHNOLOGY (Autonomous)

M.Tech. II Semester End Examinations

Model Question Paper

Course Title: ELECTRICAL DRIVES

Course Code: EE202PC

Time : 3 hours

Max. Marks : 70

Answer any FIVE Questions
(Each question carries 14 marks)

Q. No.	Stem of the question	M	L	CO	PO
Unit-I					
1. a)	Derive the transfer function of a dc motor and load	5	3	1	2
b)	Briefly explain the design of current regulator and speed controller in the feedback system?	7	2	1	2
Unit-II					
2. a)	Explain steady state analysis of chopper controlled DC motor drives by averaging	7	2	1	1
b)	What is the significance of closed loop operation and how it can be adapt to dc chopper fed drive	7	1	1	7
Unit-III					
3. a)	Explain the open loop volts/Hz control of induction motors.	7	2	2	3
b)	What is slip power? How can it be recovered? Discuss the working of Static Scherbius Drive.	7	1	4	4
Unit-IV					
4. a)	Explain the operation of induction motor when indirect method of vector control is adopted.	7	2	4	2
b)	Explain the principal of operation of Direct Torques control of induction motor drive?	7	2	4	3
Unit-V					
7. a)	Analyze the operation of constant torque mode controller in synchronous motors.	7	4	7	2
b)	Explain the unity power factor control of synchronous motors.	7	2	7	3
a. Unit-I b. Unit-II					
6. a)	Analyze the with neat block diagram different components of an electric drive.	7	4	1	3
b)	Compare stator side control and rotor side control of induction motors.	5	4	3	1
a. Unit-III b. Unit-IV					
7. a)	Explain with a neat schematic diagram, the speed control of induction motor with torque and flux control.	7	2	3	1
b)	Explain Model referencing control adaptive control technique.	7	2	4	1
a. Unit-V b. Unit-I/II/III/IV/V					
8. a)	Analyze in detail different speed control schemes for synchronous motor drives	7	4	7	4
b)	Elaborate the principal of operation of Direct Vector control of induction motor drive?	7	6	4	2

M: Marks; L: Bloom's Taxonomy Level; CO: Course Outcome; PO: Programme Outcome



MAHATMA GANDHI INSTITUTE OF TECHNOLOGY (Autonomous)

M.Tech. II Semester End Examinations

Model Question Paper

Course Title: SCADA SYSTEMS AND APPLICATIONS

Course Code: EE213PE

Time: 3 hours

Max. Marks: 70

*Answer any FIVE Questions
(Each question carries 14 marks)*

Q. No.	Stem of the question	M	L	CO	PO
Unit-I					
1. a)	Analyze Data acquisition system and its operation with block diagram	7	2	1	1
b)	Discuss the evolution of SCADA along with its features and benefits.	7	6	1	1
Unit-II					
2. a)	Define RTU and IEDs.	4	3	2	1
b)	Illustrate the programmable logic controller along with block diagram and ladder diagram,	10	2	2	2
Unit-III					
3. a)	Define IEC-61850 and its advantages and application.	7	1	2	2
b)	Explain Ethernet/IP protocol.	7	2	2	3
Unit-IV					
4. a)	Compare various communication technologies used in SCADA systems	10	4	2	4
b)	Define Modbus RTU, RP-570.	4	1	2	1
Unit-V					
5. a)	Explain automatic Substation Control through SCADA systems	10	2	3	6
b)	Interpret the case study of water treatment plant using SCADA system.	4	4	3	5
a. Unit-I b. Unit-II					
6. a)	What are the components of SCADA? Explain briefly.	7	3	1	1
b)	Explain Energy Management Systems for large interconnected power system	7	2	3	3
a. Unit-III b. Unit-IV					
7. a)	Demonstrate briefly the IOTs in SCADA systems.	4	3	1	3
b)	Explain 7 layers of OSI Model & their functions.	10	2	2	4
a. Unit-V b. Unit-I/II/III/IV/V					
8. a)	Examine SCADA system used in Petroleum Refining Process.	7	2	3	5
b)	Classify different applications of SCADA system.	7	4	3	3

M: Marks; L: Bloom's Taxonomy Level; CO: Course Outcome; PO: Programme Outcome

**MAHATMA GANDHI INSTITUTE OF TECHNOLOGY (Autonomous)****M.Tech II Semester End Examinations****Model Question Paper****Course Title: Power Quality****Course Code: EE217PE**

Time : 3 hours

Max. Marks : 70

Answer any FIVE Questions*(Each question carries 14 marks)*

Q. No.	Stem of the question	M	L	CO	PO
Unit-I					
1. a)	Examine the occurrence of transients?	7	4	1	1
b)	How the power quality monitoring is performed in Distribution systems?	7	1	1	2
Unit-II					
2. a)	Explain Evaluate the harmonic distortion in power system?	9	2	2	4
b)	How to calculate cost of interruptions?	5	2	2	3
Unit-III					
3. a)	Explain sag magnitude calculation?	7	1	3	1
b)	How sag in calculated in meshed systems?	7	1	3	1
Unit-IV					
4. a)	Explain the AC drive behavior under voltage sags?	7	2	4	1
b)	What are the mitigation methods for AC and DC drives?	7	4	4	1
Unit-V					
5. a)	Analyze the mitigation methods for voltage sag compensation?	5	4	5	2
b)	How to improve equipment immunity?	9	2	5	5
a. Unit-I b. Unit-II					
6. a)	Classify the power quality issues according to IEEE standard?	5	2	1	3
b)	Describe the reliability evolution model in power system reliability?	9	4	2	2
a. Unit-III b. Unit-IV					
7. a)	Classify sags in three-phase system based on system configuration?	6	1	3	4
b)	Discuss the voltage sag equipment behavior for Computer & consumer electronics	8	6	4	4
a. Unit-V b. Unit-I/II/III/IV/V					
8. a)	Examine about cascaded connected voltage controllers?	7	4	5	3
b)	What is voltage sag equipment behavior for Power electronic devices?	7	1	4	4

M: Marks; L: Bloom's Taxonomy Level; CO: Course Outcome; PO: Programme Outcome